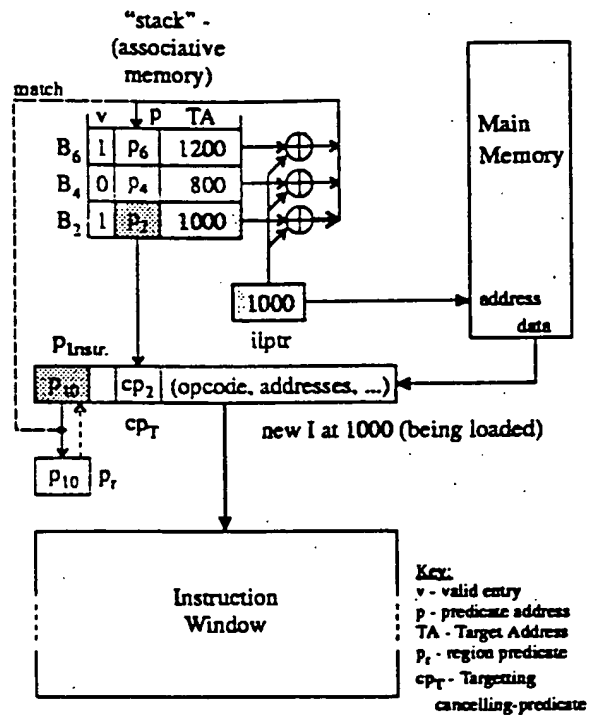Disjoint   Nested   Overlapped

FIG. 1

Snapshot taken at t = 9+ of Example 5.
- new I matches target address in stack

FIG. 2

load time	address	code		predicate-assignment (at load time)					predicate-use (at code execution time)		
				stack				$p_{in}=p_r$	cp_{in}	p_{out}	cp_{out}	p_I - condition for I execution
				B	v	p	TA					
1	100	I_1	$z = x\ op\ y$			empty		1	0	$p_1=1$	-	1
2	200	B_2	if (bc_2) goto 400	B_2	1	P_2	400	1	0	$p_2=\overline{bc}_2$	bc_2	1
3	300	I_3		B_2	1	P_2	400	P_2	0	-	-	$\overline{bc}_2$
4	400	I_4				empty		P_2	cp_2	$\overline{bc}_2+bc_2$	-	$\overline{bc}_2+bc_2=1$
5	500	I_5				empty		P_4	0	-	-	$p_4=1$
6	600	B_6	if (bc_6) goto 800	B_6	1	P_6	800	P_4	0	$\overline{bc}_6{\cdot}P_4$	$bc_6{\cdot}P_4$	1
7	700	I_7		B_6	1	P_6	800	P_6	0	-	-	$\overline{bc}_6$
8	800	I_8				empty		P_6	cp_6	$\overline{bc}_6+bc_6$	-	$\overline{bc}_6+bc_6=1$
9	900	I_9				empty		P_8	0	-	-	$p_6=1$

Equations - for "T": $p_I=p_{out}=p_{in}+cp_{in}$; for "B": $p_{out}=\overline{bc}{\cdot}p_{in}$, $cp_{out}=bc{\cdot}p_{in}$

FIG. 3

				predicate-assignment (at load time)				predicate-use (at code execution time)		
				stack						
load time	address	code		B v p TA	$p_{in}=p_f$	cp_{in}	p_{out}	cp_{out}	p_I - condition for I execution	
1	100	I_1	z = x op y	empty	1	0	$p_1=1$	-	1	
2	200	B_2	if (bc_2) goto 800	B_2 1 P_2 800	1	0	$p_2=\overline{bc_2}$	bc_2	1	
3	300	I_3		B_2 1 P_2 800	P_2	0	-	-	$\overline{bc_2}$	
4	400	B_4	if (bc_4) goto 600	B_4 1 P_4 600 B_2 1 P_2 800	P_2	0	$\overline{bc_4}{\cdot}P_2$	$bc_4{\cdot}P_2$	1	
5	500	I_5		B_4 1 P_4 600 B_2 1 P_2 800	P_4	0	-	-	$\overline{bc_2}{\cdot}\overline{bc_4}$	
6	600	I_6		B_2 1 P_2 800	P_4	cp_4	P_4+cp_4	-	$\overline{bc_4}{\cdot}\overline{bc_2}+bc_4{\cdot}\overline{bc_2}=\overline{bc_2}$	
7	700	I_7		B_2 1 P_2 800	P_6	0	-	-	$\overline{bc_2}$	
8	800	I_8		empty	P_6	cp_2	P_6+cp_2	-	$\overline{bc_2}+bc_2=1$	
9	900	I_9		empty	P_8	0	-	-	1	

Equations -   for "I": $p_I=p_{out}=p_{in}+cp_{in}$;   for "B": $p_{out}=\overline{bc}{\cdot}p_{in}$, $cp_{out}=bc{\cdot}p_{in}$

FIG. 4

				predicate-assignment (at load time)					predicate-use (at code execution time)		
				stack							
load time	address	code		B	v	p	TA	$p_{in}=p_r$	cp_{in}	p_{out}	cp_{out}	p_I - condition for I execution
1	100	I_1	z = x op y		empty			1	0	$p_1=1$	--	1
2	200	B_2	if (bc_2) goto 600	B_2	1	P_2	600	1	0	$p_2=\overline{bc}_2$	bc_2	1
3	300	I_3		B_2	1	P_2	600	P_2	0	-	-	$\overline{bc}_2$
4	400	B_4	if (bc_4) goto 800	B_4	1	P_4	800	P_2	0	$\overline{bc}_4{\cdot}P_2$	$bc_4{\cdot}P_2$	1
				B_2	1	P_2	600					
5	500	I_5		B_4	1	P_4	800	P_4	0	-	-	$\overline{bc}_4{\cdot}\overline{bc}_2$
				B_2	1	P_2	600					
6	600	I_6		B_4	1	P_4	800	P_4	cp_2	P_4+cp_2	-	$(\overline{bc}_4{\cdot}\overline{bc}_2)+bc_2=\overline{bc}_4+bc_2$
				B_2	0	P_2	600					
7	700	I_7		B_4	1	P_4	800	P_6	0	-	-	$\overline{bc}_4+bc_2$
				B_2	0	P_2	600					
8	800	I_8			empty			P_6	cp_4	P_6+cp_4	-	$\overline{bc}_4+bc_2+(bc_4{\cdot}\overline{bc}_2)=1$
9	900	I_9			empty			P_8	0	-	-	1

Equations -   for "T": $p_I=p_{out}=p_{in}+cp_{in}$;   for "B": $p_{out}=\overline{bc}{\cdot}p_{in}$, $cp_{out}=bc{\cdot}p_{in}$

FIG. 5

				predicate-assignment (at load time)					predicate-use (at code execution time)		
				stack							
load time	address	code		B	v	p	TA	$p_{in}=p_r$	cp_{in}	p_{out}	cp_{out}	p_I - condition for I execution
1	100	I_1	z = x op y			empty		1	0	$p_1=1$	-	1
2	200	B_2	if (bc$_2$) goto 1000	B_2	1	p_2	1000	1	0	$p_2=\overline{bc_2}$	bc_2	1
3	300	I_3		B_2	1	p_2	1000	p_2	0	-	-	$\overline{bc_2}$
4	400	B_4	if (bc$_4$) goto 800	B_4	1	p_4	800	p_2	0	$\overline{bc_4}\cdot p_2$	$bc_4\cdot p_2$	1
				B_2	1	p_2	1000					
5	500	I_5		B_4	1	p_4	800	p_4	0	-	-	$\overline{bc_4}\cdot\overline{bc_2}$
				B_2	1	p_2	1000					
6	600	B_6	if (bc$_6$) goto 1200	B_6	1	p_6	1200	p_4	0	$\overline{bc_6}\cdot p_4$	$bc_6\cdot p_4$	1
				B_4	1	p_4	800					
				B_2	1	p_2	1000					
7	700	I_7		B_6	1	p_6	1200	p_6	0	-	-	$\overline{bc_6}\cdot\overline{bc_4}\cdot\overline{bc_2}$
				B_4	1	p_4	800					
				B_2	1	p_2	1000					
8	800	I_8		B_6	1	p_6	1200	p_6	cp_4	p_6+cp_4	-	$(\overline{bc_6}\cdot\overline{bc_4}\cdot\overline{bc_2})+(bc_4\cdot\overline{bc_2})$ $=(\overline{bc_6}+bc_4)\overline{bc_2}$
				B_4	0	p_4	800					
				B_2	1	p_2	1000					
9	900	I_9		B_6	1	p_6	1200	p_8	0	-	-	$(\overline{bc_6}+bc_4)\overline{bc_2}$
				B_4	0	p_4	800					
				B_2	1	p_2	1000					
10	1000	I_{10}		B_6	1	p_6	1200	p_8	cp_2	p_8+cp_2	-	$((\overline{bc_6}+bc_4)\overline{bc_2})+bc_2$ $=\overline{bc_6}+bc_4+bc_2$
11	1100	I_{11}		B_6	1	p_6	1200	p_{10}	0	-	-	$\overline{bc_6}+bc_4+bc_2$
12	1200	I_{12}				empty		p_{10}	cp_6	$p_{10}+cp_6$	-	$\overline{bc_6}+bc_4+bc_2+(bc_6\cdot\overline{bc_4}\cdot\overline{bc_2})$ $=1$
13	1300	I_{13}				empty		p_{12}	0	-	-	1

Equations -   for "I": $p_I=p_{out}=p_{in}+cp_{in}$;   for "B": $p_{out}=\overline{bc}\cdot p_{in}$, $cp_{out}=bc\cdot p_{in}$

FIG. 6